



CENG 232 - Logisim

Middle East Technical University

Department of Computer Engineering

LOGISIM


- ▶ Tool for designing and simulating digital logic circuits
- ▶ Drag and drop GUI
- ▶ Provides gates and the integrated circuits

LOGISIM

- ▶ Should be downloaded from ODTUClass course page.
(logisim.jar)
- ▶ Logisim used in this course is a modified version.
- ▶ **DO NOT USE ANY OTHER VERSION!**
Only use logisim.jar which is given in OdtuClass.
- ▶ **Otherwise, grading will not be possible!**

LOGISIM

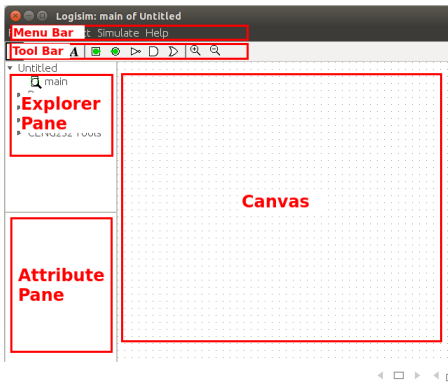
- ▶ Java: Works on Windows/Linux/Mac
- ▶ In Linux you can run with:
"java -jar logisim.jar"
- ▶ For other platforms, just double click to open.
- ▶ Java must be installed.



HOW TO START


- ▶ Example problem:
 - ▶ Design XOR using **and**, **or** and **not** gates.
- ▶ Design circuit on paper.
- ▶ Decide how will you draw (shape).

x	y	$x \text{ XOR } y$
0	0	0
0	1	1
1	0	1
1	1	0

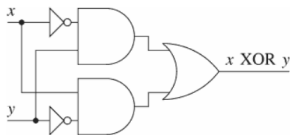


ADDING GATES

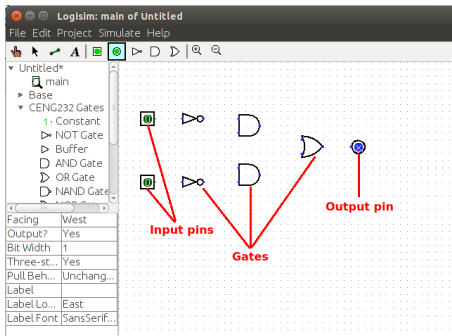- ▶ First, add gates to build a skeleton.
- ▶ Find, Ceng232 Gates from explorer pane.
- ▶ Choose the appropriate gate and click on canvas.
- ▶ To add more than one of the same gate, just continue clicking on canvas.
- ▶ *Input Pins* and *Output Pins* should be added from tool bar at the top. Do not add *pins* from elsewhere.




CHANGING ATTRIBUTES

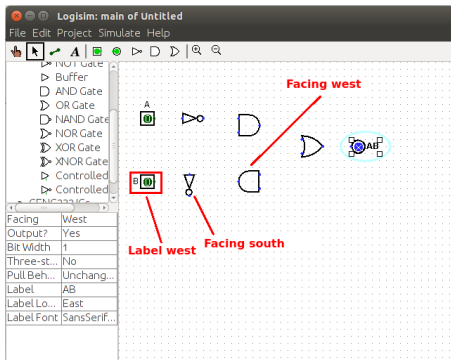- ▶ Is done by using the attributes pane.
- ▶ *Facing* attribute sets the direction you connect cables.
- ▶ You can add a *Label* to give input and output pins a name.
- ▶ Attributes of gates can only be changed before adding it to canvas.




ADDING WIRES

- ▶ Select the wiring tool from tool bar.
- ▶ Drag from one position to another in the canvas area, and a wire will start to appear between the two points.
- ▶ Wires in Logisim must be horizontal or vertical.
- ▶ Logisim automatically draws the circle at a wire intersection to indicate wires are connected.
- ▶ Blue in Logisim indicates that the value at that point is *unknown*, and gray indicates that the wire is not connected to anything.

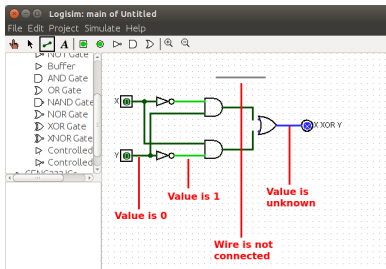


TESTING YOUR CIRCUIT

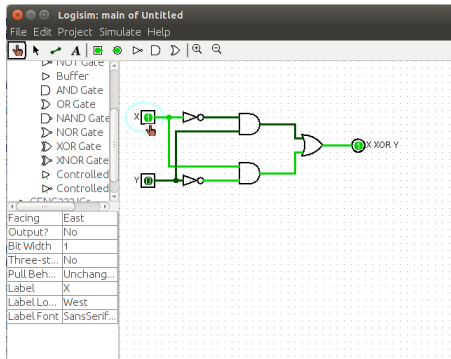- ▶ Select poke tool from tool bar.
- ▶ Start poking the inputs by clicking on them.
- ▶ Each time you poke an input, its value will toggle.



PLA STYLE

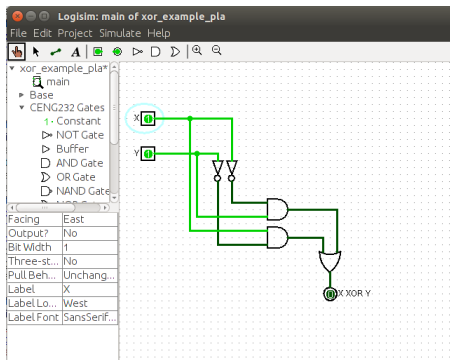
- ▶ PLA = Programmable Logic Array
 - ▶ A topic that will be covered in the class later.
- ▶ Make a 90 degree turn before adding each level of gates.
- ▶ More readable and useful when the circuit is large.



FOR THE LABS


- ▶ Label each input and output correctly with the names described in the homework text.
- ▶ Generate all outputs by building one circuit (do not build a circuit for each of the outputs !).
- ▶ Do not duplicate labels (all labels should be used exactly once).

FOR THE LABS - DON'TS

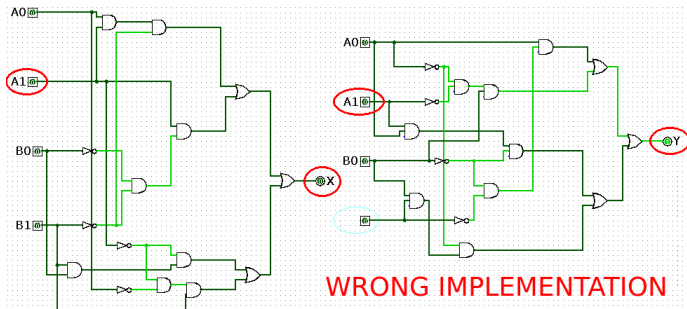

- ▶ DON'T create duplicate (same name) input and output pins.
- ▶ DON'T build separate circuits to provide multiple outputs.
- ▶ DON'T forget to label each input pin.
- ▶ DON'T use gates apart from CENG232 gates and CENG232 ICs.
- ▶ DON'T add a label unless it is specifically wanted.

FOR THE LABS - DO'S

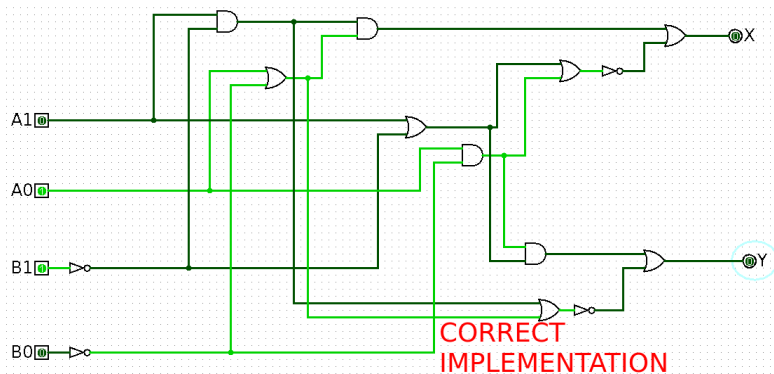

- ▶ Label each input and output.
- ▶ Generate a single circuit for all of the outputs.
- ▶ Minimize the circuit (use less number of gates).
- ▶ Only use the gates allowed for you in that assignment.

NOTES

- ▶ **Black-box testing:**
 - ▶ Be careful with labeling.
 - ▶ Labels are case sensitive.
 - ▶ i.e.: A label "A0" is not the same label as "a0" or "A_0".

LINKS AND TOOLS

- ▶ Logisim CENG232 version:
 - ▶ You can download from ODTUClass course page.
 - ▶ Use the provided version only, any other versions won't be graded!